

# ELC 2137 Lab 05: Verilog Intro

My Nguyen

September 30, 2020

## Summary

This lab purpose is to learn the basic Verilog syntax, organize files and folder structure to recreate half-adder, full-adder, and 2-bit adder/subtractor. First, familiarize by creating a RTL project using Basys3 board. From this create a half-adder file and populate it with code and logic for a half-adder, then create a test file to exhaustively test it. Repeat this process for full-adder and 2-bit adder/subtractor.

## Table and Figure

## Code

Listing 1: Half Adder Implementation

---

```
module half_adder(  
    input a,  
    input b,  
    output c,  
    output s  
);  
    assign c = a & b; // can't use "s" to calculate "c"  
    assign s = a ^ b; // everything is one directional  
endmodule
```

---

Listing 2: Half Adder Test Bench

---

```
module half_adder_test();  
    //input -> reg , ouput -> wire  
    reg a;  
    reg b;  
    wire c;  
    wire s;  
  
    half_adder dut(  
        .a(a),  
        .b(b),  
        .c(c),  
        .s(s)  
    );  
    initial begin  
        a=0; b=0; #10;  
        a=1; b=0; #10;  
        a=0; b=1; #10;  
    end
```

---

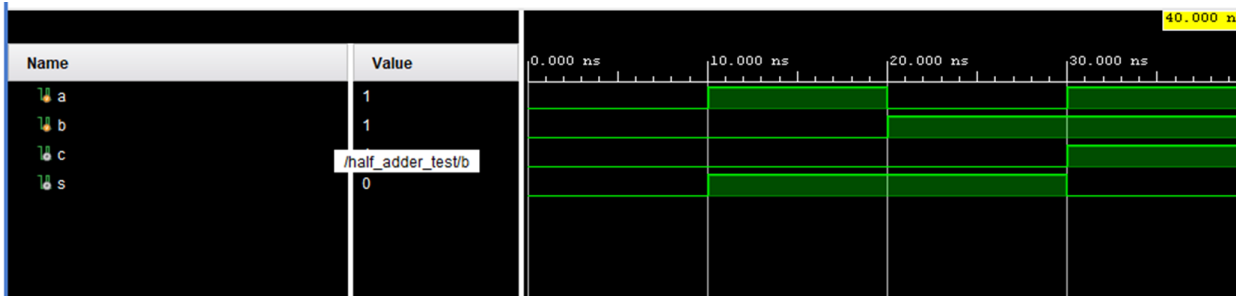


Figure 1: Half Adder ERT

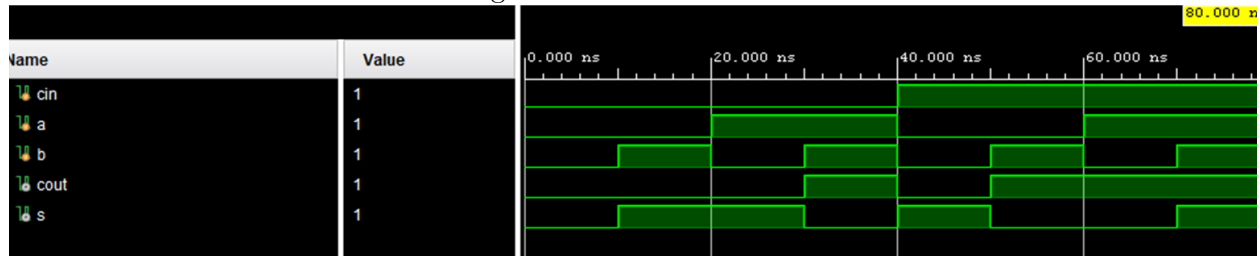


Figure 2: Full Adder ERT



Figure 3: 2-bit Adder/Subtractor ERT

```

a=1; b=1; #10;

$finish;
end
endmodule

```

Listing 3: Full Adder Implementation

```

module full_adder(
    input a,
    input b,
    input cin,
    output cout,
    output s
);

```

```

//internal signals
wire c1, c2, s1;

//first half adder
half_adder ha0(
    .a(a),
    .b(b),
    .c(c1),
    .s(s1)
);

//second half adder
half_adder ha1(
    .a(s1),
    .b(cin),
    .c(c2),
    .s(s)
);

//the last xor gate connecting cin and the second carry
assign cout = c1 ^ c2;

endmodule

```

---

Listing 4: Full Adder Test Bench

---

```

module full_adder_test();
    reg cin;
    reg a;
    reg b;
    wire cout;
    wire s;

    //initilize a full adder for testing
    full_adder dut(
        .a(a),
        .b(b),
        .cin(cin),
        .cout(cout),
        .s(s)
    );

    //test cases
    initial begin
        cin = 0; a = 0; b = 0; #10;
        cin = 0; a = 0; b = 1; #10;
        cin = 0; a = 1; b = 0; #10;
        cin = 0; a = 1; b = 1; #10;
        cin = 1; a = 0; b = 0; #10;
        cin = 1; a = 0; b = 1; #10;
        cin = 1; a = 1; b = 0; #10;
        cin = 1; a = 1; b = 1; #10;
        $finish;
    end
endmodule

```

```
end  
endmodule
```

---

Listing 5: 2-bit Adder/Subtractor Implementation

---

```
module adder_subtractor(  
    input [1:0] a, b,  
    input mode,  
    output cbout,  
    output [1:0] sum  
);  
  
    wire c1, c2;  
    wire [1:0] b_add;  
  
    //Invert b input for subtraction  
    assign b_add[0] = b[0] ^ mode;  
    assign b_add[1] = b[1] ^ mode;  
  
    //the first full adder  
    full_adder fa0(  
        .a(a[0]),  
        .b(b_add[0]),  
        .cin(mode),  
        .cout(c1),  
        .s(sum[0])  
    );  
  
    //the second full adder  
    full_adder fa1(  
        .a(a[1]),  
        .b(b_add[1]),  
        .cin(c1),  
        .cout(c2),  
        .s(sum[1])  
    );  
  
    //Convert carry to borrow when subtracting  
    assign cbout = c2 ^ mode;  
endmodule
```

---

Listing 6: 2-bit Adder/Subtractor Test Bench

---

```
module adder_subtractor_test();  
    reg [1:0] a, b;  
    reg mode;  
    wire [1:0] sum;  
    wire cbout;  
  
    adder_subtractor dut(  
        .a(a),  
        .b(b),  
        .mode(mode),  
        .cbout(cbout),  
    );  
endmodule
```

```

        .sum(sum)
    );

    //test cases for addition and subtraction
    initial begin
        mode = 0; a[1] = 0; a[0] = 0; b[1] = 0; b[0] = 1; #10;
        mode = 0; a[1] = 0; a[0] = 0; b[1] = 1; b[0] = 0; #10;
        mode = 0; a[1] = 0; a[0] = 0; b[1] = 1; b[0] = 1; #10;
        mode = 0; a[1] = 0; a[0] = 1; b[1] = 0; b[0] = 1; #10;
        mode = 0; a[1] = 1; a[0] = 0; b[1] = 0; b[0] = 1; #10;
        mode = 0; a[1] = 1; a[0] = 0; b[1] = 0; b[0] = 0; #10;

        mode = 1; a[1] = 0; a[0] = 0; b[1] = 0; b[0] = 1; #10;
        mode = 1; a[1] = 0; a[0] = 0; b[1] = 1; b[0] = 0; #10;
        mode = 1; a[1] = 0; a[0] = 0; b[1] = 1; b[0] = 1; #10;
        mode = 1; a[1] = 0; a[0] = 1; b[1] = 0; b[0] = 1; #10;
        mode = 1; a[1] = 1; a[0] = 0; b[1] = 0; b[0] = 1; #10;
        mode = 1; a[1] = 1; a[0] = 0; b[1] = 0; b[0] = 0; #10;

        $finish;
    end
endmodule

```

---

## Screenshot

## Questions

4. The simulations matches exact the result from lab 3 and lab 4. 5. One thing I still cannot figure out is how to assign value to a multi-bit variable using another multi-bit variable.

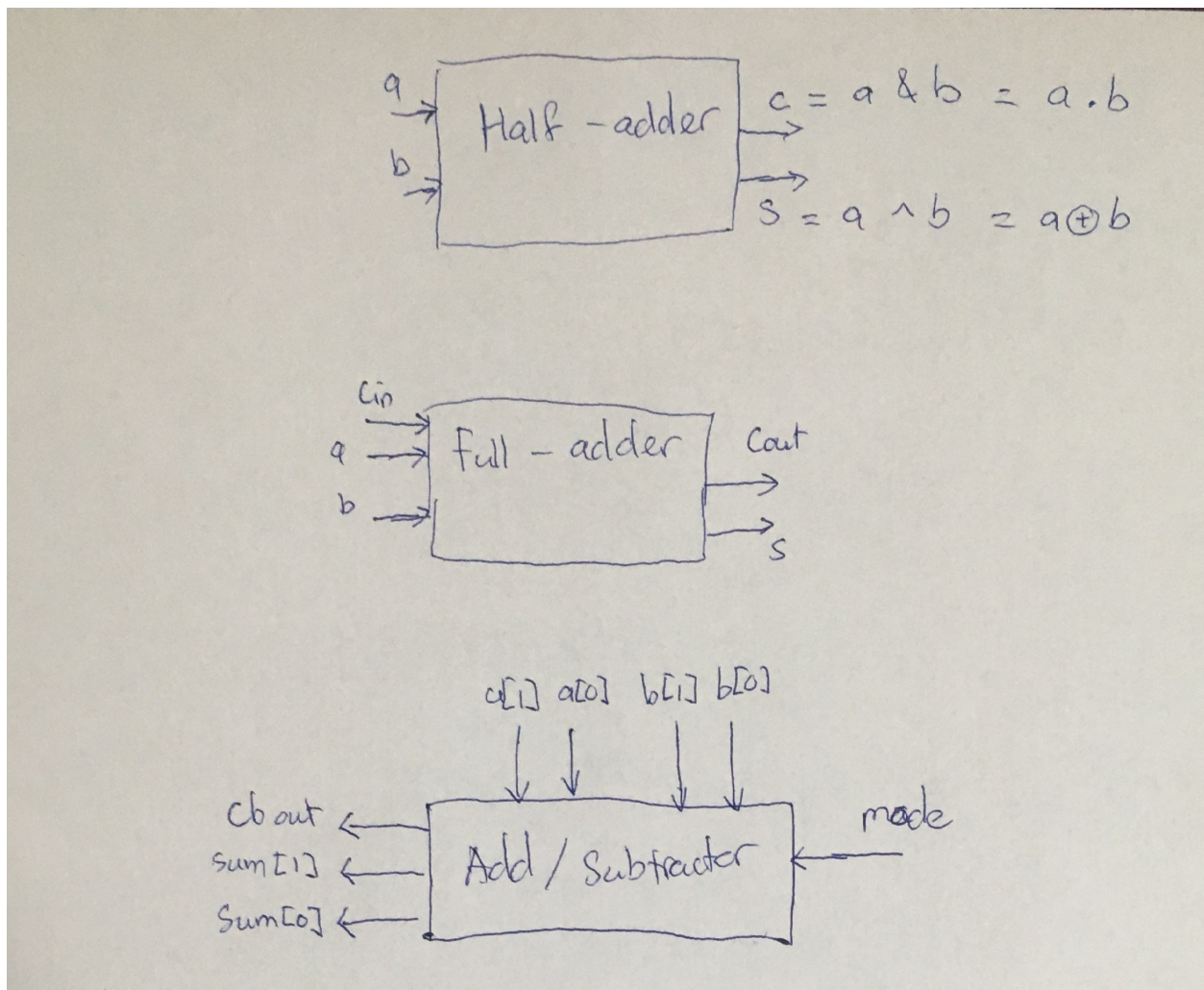


Figure 4: Block Diagrams